

EEL 4837

Programming for Electrical Engineers II

Qiangeng Yang
Teaching Assistant

Department of Electrical and Computer Engineering
University of Florida at Gainesville


Excursion 1 – Circuit Analysis Tool

Readings:

- Excursion 1 Description


Electronic Circuit

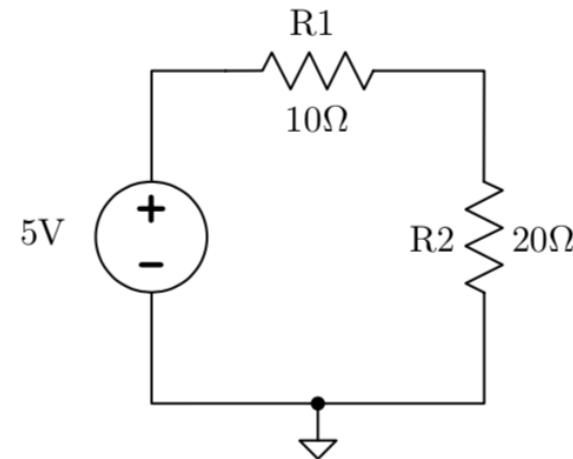- **Electronic circuit:** a collection of interconnected electronic components.
- A circuit has a well-defined deterministic functionality when running:
 - Voltage sources
 - Current sources
 - Resistors
 - Inductors
 - Capacitors
 - Diodes
 - Transistors
 - ...



Electronic Circuit (cont.)

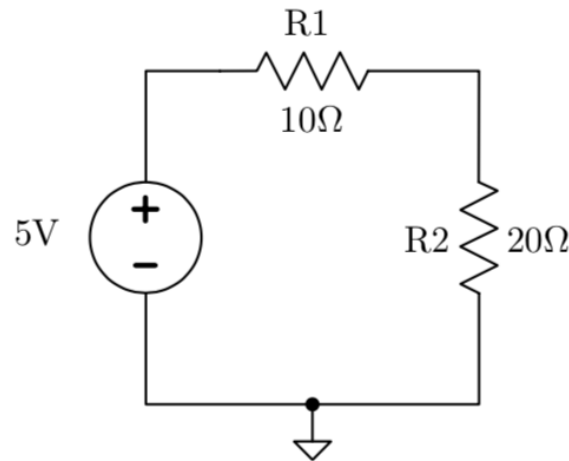- The functionality of a circuit is fully characterized by:
 - The **current** through each component.
 - The **voltage drop/rise** through each component.
 - The **voltage potential** at each of the interconnections relative to a ground node.




Circuit Analysis

- **Circuit analysis:** a sequence of methods to answer some questions about circuit.
 - e.g., what is the voltage drop/rise across a resistor?
- To do that, we may need:
 - Measuring tools.
 - e.g., Galvanometer, voltmeter, ohmmeter, etc.
 - Theories.
 - e.g., Ohm's Law, Voltage Law, Current Law, etc.
- Limitations:
 - Sometimes we can only answer questions as needed about the circuit at a time.

Circuit Simulation


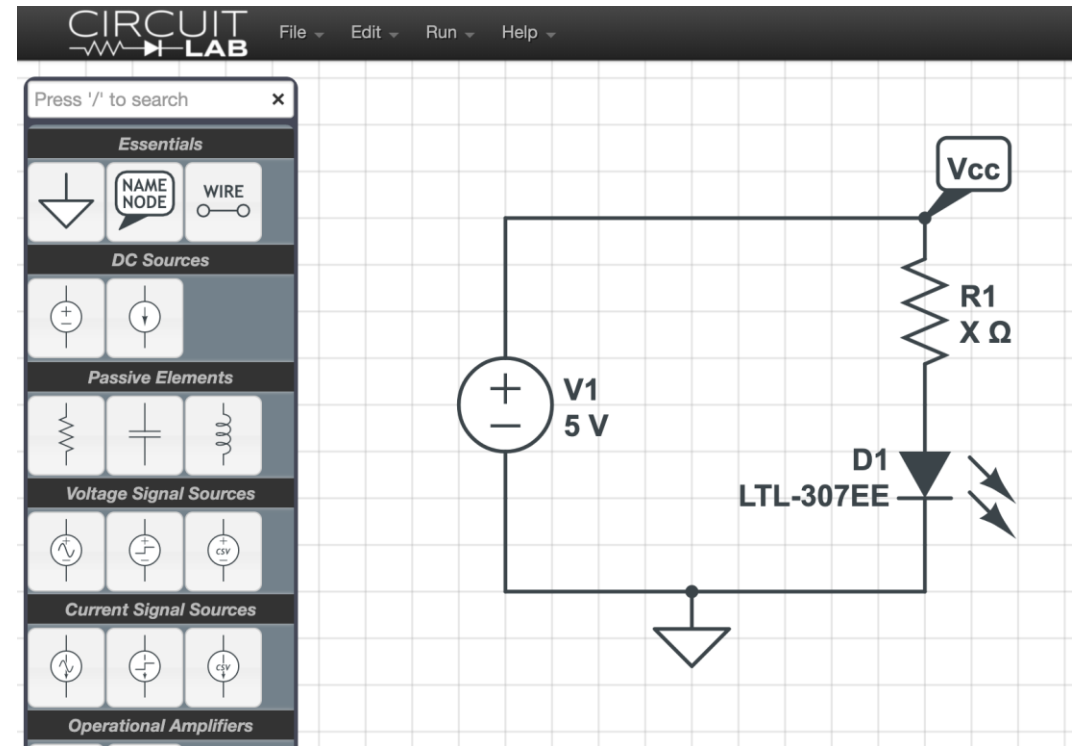
- **Circuit simulation:** a technique to check and verify the design of circuits prior to manufacturing and deployment.
- Almost replaced physical prototype.
- What can we do with simulation?
 - Model a linear circuit with a single matrix algebraic equation.



From: [CircuitLab](#)



Schematic Diagrams and Digraphs

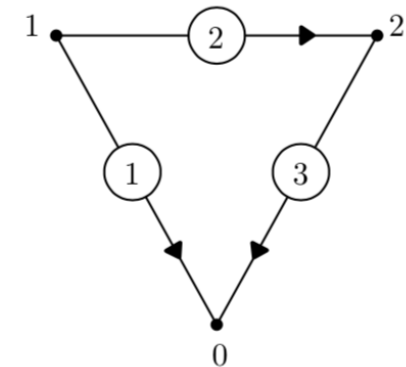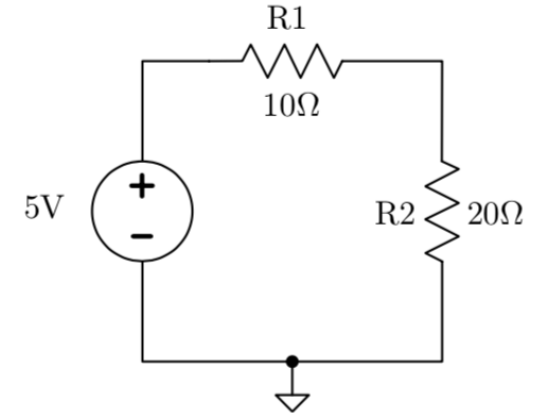- **Schematic diagram:** a graphical representation of an electrical circuit.
- **Directed graph (digraph):** can represent a circuit more abstractly.
 - From graph theory.



Circuit Netlist

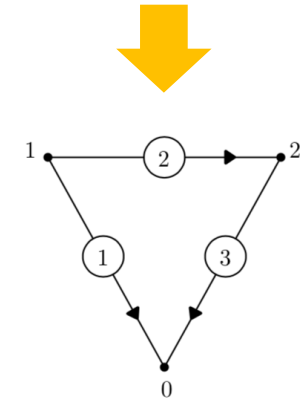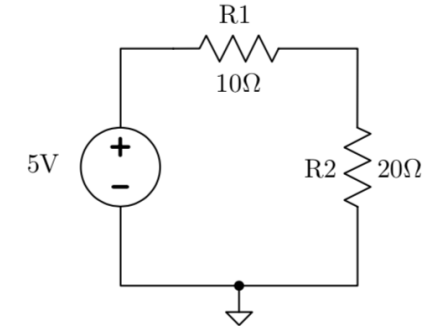
- **Netlist:** describes the connectivity of an electronic circuit.
- It consists of:
 - a list of **electronic components**;
 - a list of **nodes** they are connected to.
- **Format:**
 - Branch label
 - First character indicates component type.
 - Source node label
 - Destination node label
 - Numeric component value



V1	1	0	5
R1	1	2	10
R2	2	0	20

Circuit Netlist

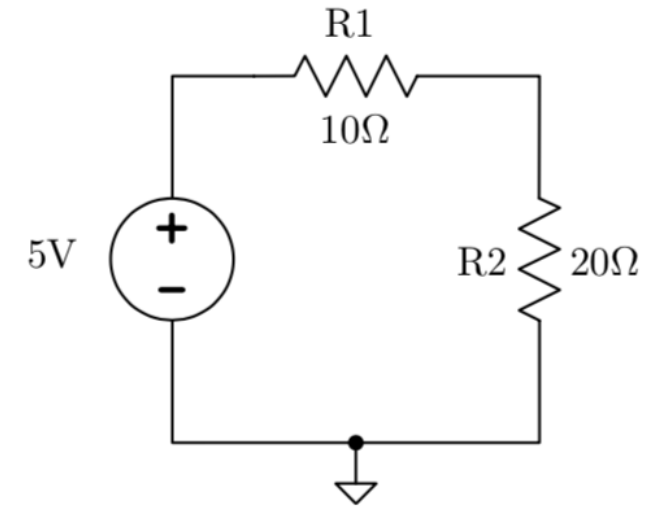
- Some conventions:
 - Ground node is always labeled as 0, while other node can be labeled in any order.
 - Use positive numeric values.
 - Current travels from source to destination.
 - Voltage drops from source to destination.



V1	1	0	5
R1	1	2	10
R2	2	0	20

Circuit in Computer

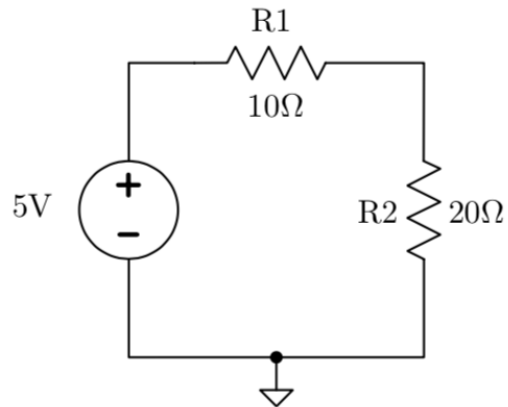- How can we represent a circuit in computer?



Circuit Diagram

V1 1 0 5
R1 1 2 10
R2 2 0 20

Netlist

$$\begin{bmatrix} \mathbf{0} & \mathbf{0} & \mathbf{A} \\ -\mathbf{A}^T & \mathbf{1} & \mathbf{0} \\ \mathbf{0} & \mathbf{M} & \mathbf{N} \end{bmatrix} \begin{bmatrix} \mathbf{e} \\ \mathbf{v} \\ \mathbf{i} \end{bmatrix} = \begin{bmatrix} \mathbf{0} \\ \mathbf{0} \\ \mathbf{u}_s \end{bmatrix}$$

Matrix

Excursion 1 Goal


- Design an elementary interactive circuit analysis tool to:
 - Read a circuit.
 - Compute the currents and voltages across different components.
- You can assume that the given circuits only contain:
 - voltage sources
 - resistors

Steps Overview

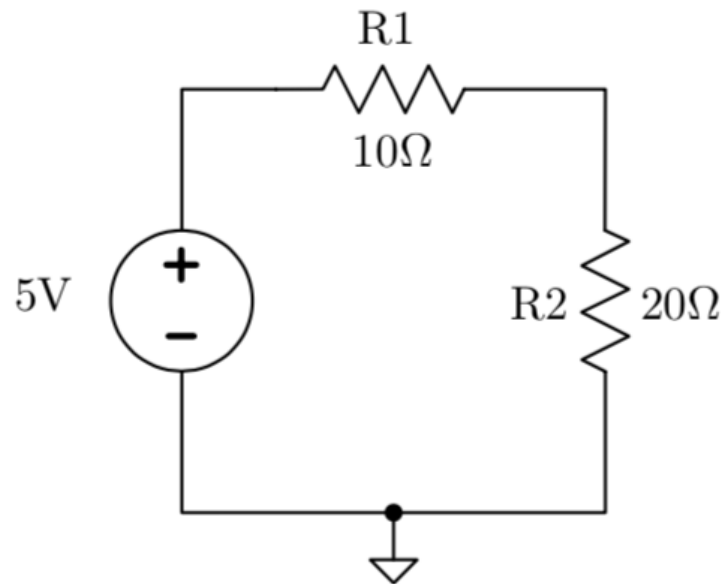1. Create a netlist as input to represent a circuit.
2. Use KCL, KVL and Ohm's law to construct three matrix equations.
3. Combine all the matrix equations to solve all the unknown parameters (e , v , i of each part).

Step 1: Create a Netlist

- Based on a circuit diagram, create its corresponding netlist as input.



V1	1	0	5
R1	1	2	10
R2	2	0	20

Step 2: From Netlist to Matrix

- How can we represent the netlist in computer?

V1	1	0	5
R1	1	2	10
R2	2	0	20





$$A_a = \begin{matrix} & n_0 & \begin{bmatrix} -1 & 0 & -1 \end{bmatrix} \\ \begin{matrix} n_1 \\ n_2 \end{matrix} & \begin{bmatrix} 1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \end{matrix} \begin{matrix} \text{node} \\ \text{branch} \end{matrix}$$

b_1 b_2 b_3

Assume “1” is source and “-1” is destination.

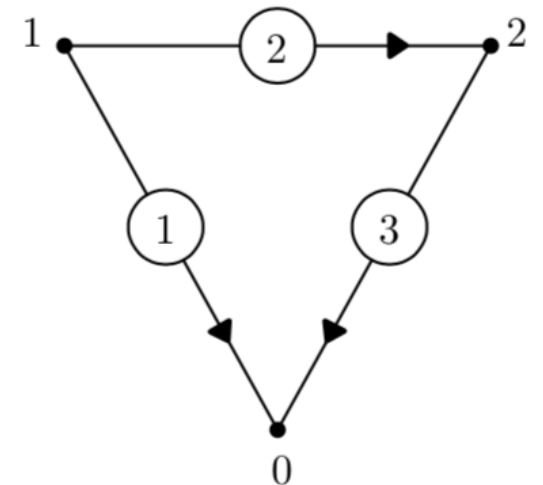
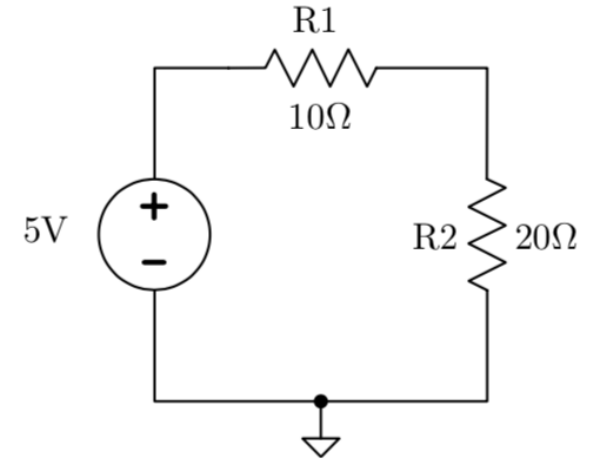
In each column, we put a “1” in the source node row and “-1” in the destination node row.



Step 2: From Netlist to Matrix



- (Cont.) We can further remove the row for one node (e.g., ground node) to get a reduced incidence matrix.
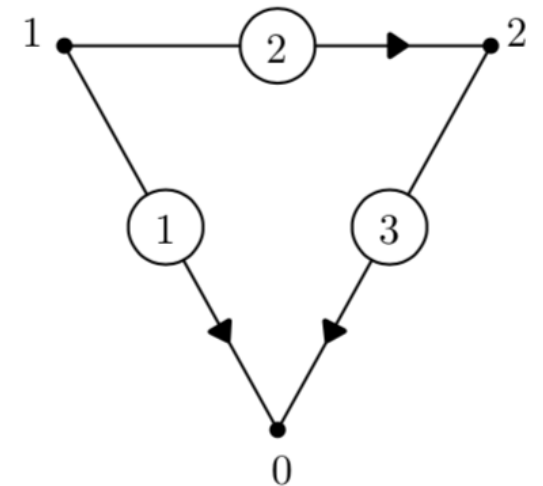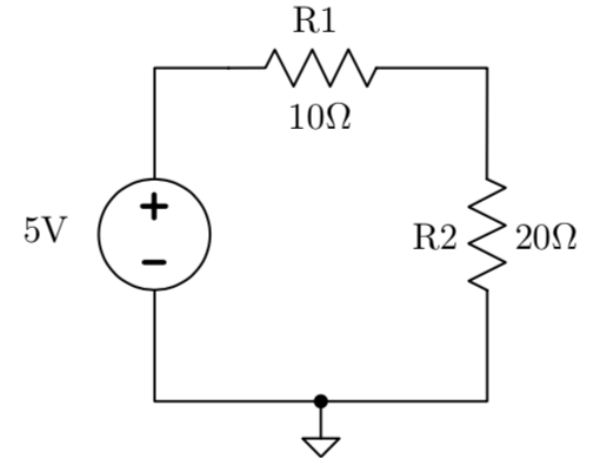
$$A_a = \begin{matrix} & \cancel{n_0} \\ n_1 & \begin{bmatrix} -1 & 0 & -1 \end{bmatrix} \\ n_2 & \begin{bmatrix} 1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \end{matrix} \begin{matrix} \\ b_1 \\ b_2 \\ b_3 \end{matrix} \Rightarrow A = \begin{bmatrix} 1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix}$$



Step 2: From Netlist to Matrix

- **Kirchoff's Current Law (KCL):** the algebraic sum of currents that leave any node is zero.
- KCL equation for each node:
 - Assume leaving is positive and coming is negative:
 - At Node 0: branch currents i_1 and i_3 are coming, so
$$-i_1 - i_3 = 0$$
 - At Node 1: branch currents i_1 and i_2 are leaving, so
$$i_1 + i_2 = 0$$
 - At Node 2: branch current i_2 is coming, while i_3 is leaving, so
$$-i_2 + i_3 = 0$$

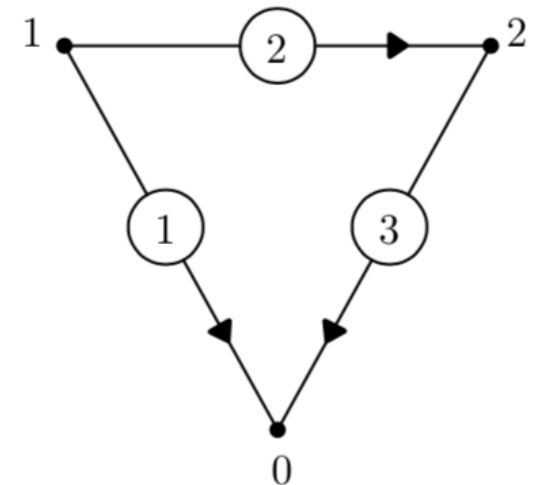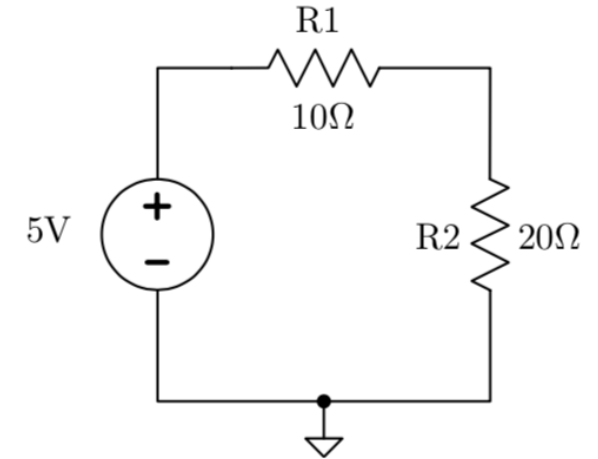

Step 2: From Netlist to Matrix

- (Cont.) Now we have:



$$-i_1 - i_3 = 0$$

$$i_1 + i_2 = 0$$

$$-i_2 + i_3 = 0$$



- Represent these equations with matrices:
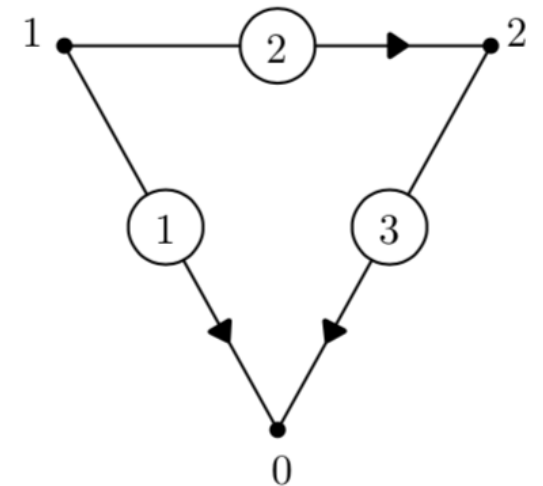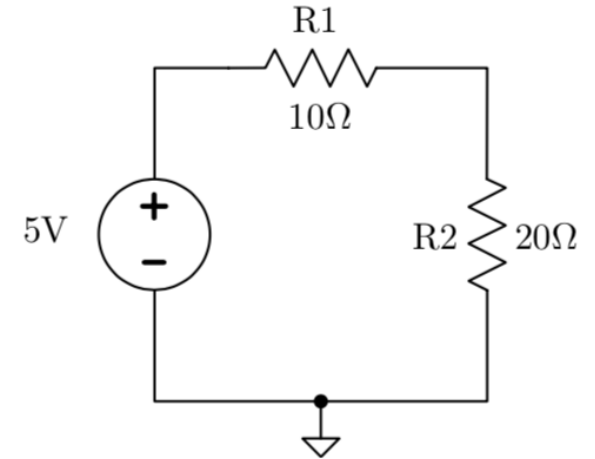
$$\begin{bmatrix} -1 & 0 & -1 \\ 1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix} \quad \Rightarrow \quad \mathbf{A}\mathbf{i} = \mathbf{0}$$



Step 2: From Netlist to Matrix

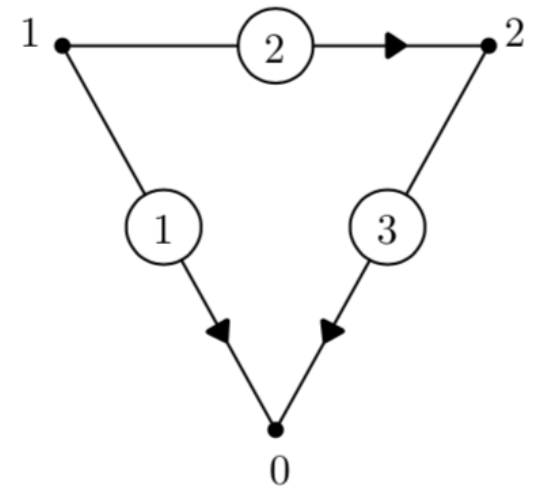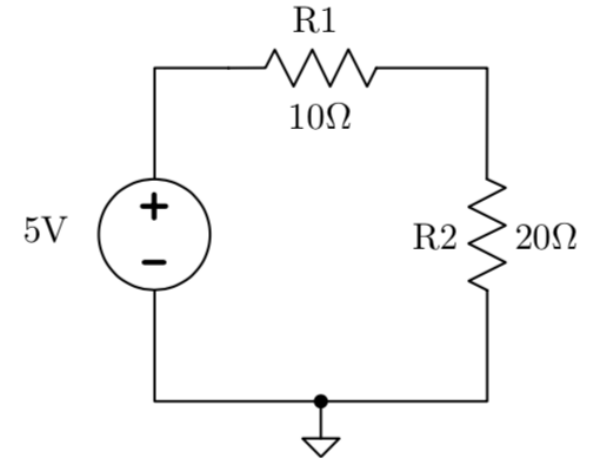- **Kirchhoff's Voltage Law (KVL):** the voltage drop between any two nodes is equal to the difference of the two node voltages.
- KVL equation for each pair of nodes:
 - Voltage drop between n_0 and n_1 (branch 1):
$$v_1 = e_1 - 0$$
 - Voltage drop between n_1 and n_2 (branch 2):
$$v_2 = e_1 - e_2$$
 - Voltage drop between n_0 and n_2 (branch 3):
$$v_3 = e_2 - 0$$



Step 2: From Netlist to Matrix

- (Cont.) Now we have:



$$v_1 = e_1 - 0$$

$$v_2 = e_1 - e_2$$

$$v_3 = e_2 - 0$$

- Represent these equations with matrices:
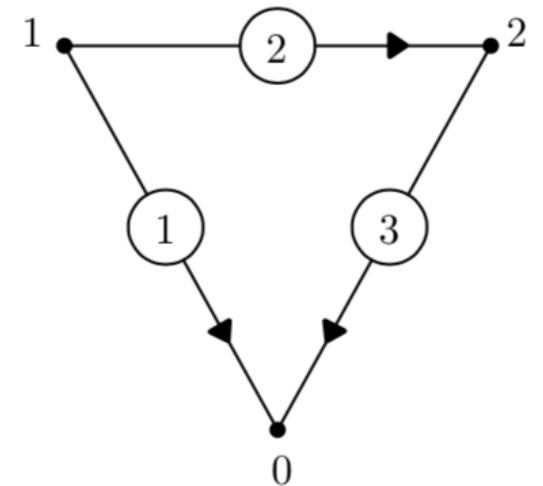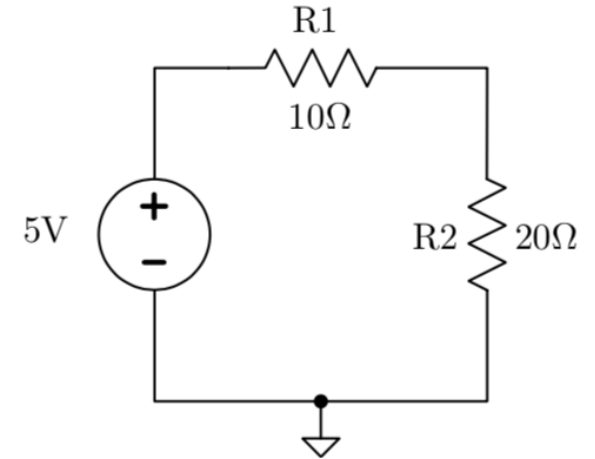
$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 1 & -1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} \quad \Rightarrow \quad \mathbf{v} = \mathbf{A}^T \mathbf{e}$$



Step 2: From Netlist to Matrix

- Comparison between KCL and KVL:

KCL



$$\begin{bmatrix} -1 & 0 & -1 \\ 1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

$$A\mathbf{i} = \mathbf{0}$$

KVL

$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 1 & -1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix}$$

$$\mathbf{v} = \mathbf{A}^T \mathbf{e}$$

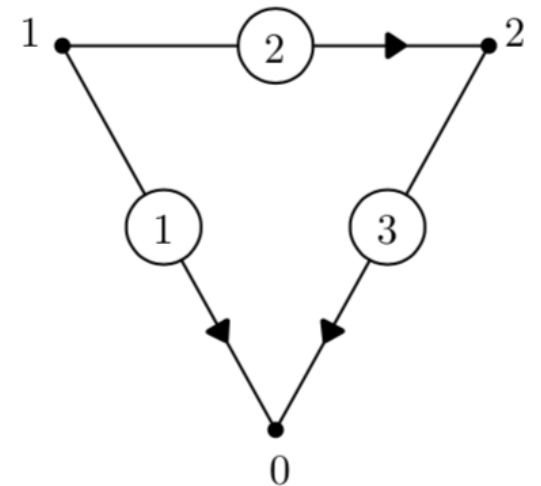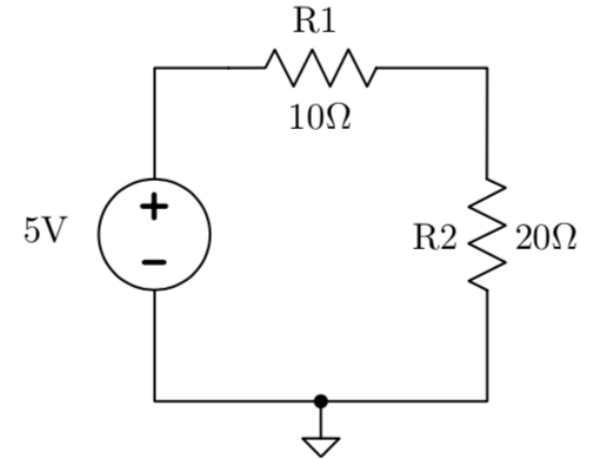

Step 2: From Netlist to Matrix



- Combine the KCL and KVL equations:

$$Ai = 0$$

$$v = A^T e$$


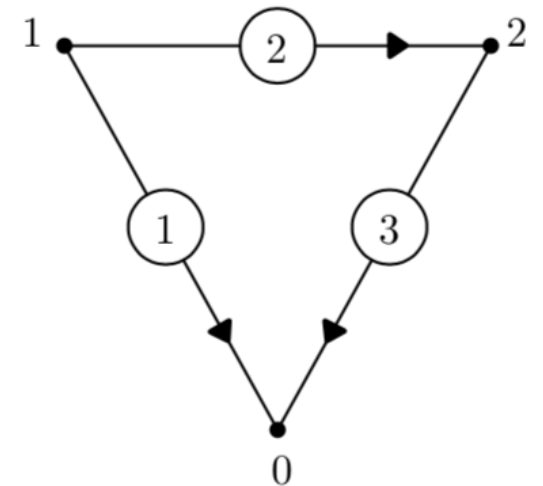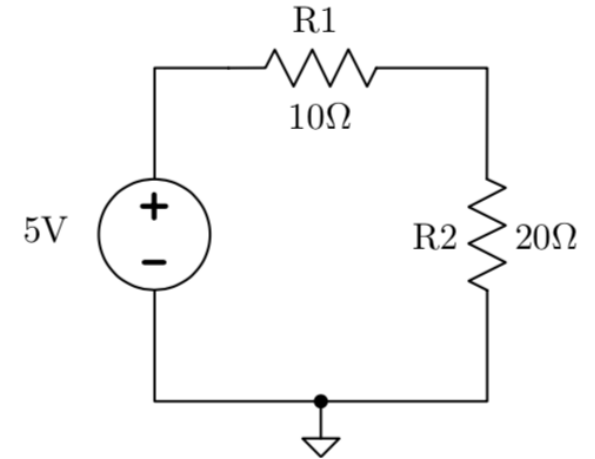
$$\begin{bmatrix} \mathbf{0} & \mathbf{0} & A \\ -A^T & \mathbf{1} & \mathbf{0} \end{bmatrix} \begin{bmatrix} e \\ v \\ i \end{bmatrix} = \begin{bmatrix} \mathbf{0} \\ \mathbf{0} \end{bmatrix}$$



Step 2: From Netlist to Matrix

- **Ohm's law:** the current through a conductor between two points is directly proportional to the voltage across the two points.



- $I = \frac{V}{R}$

- Ohm's law equation for each component:

$$v_1 = 5$$

$$v_2 = 10i_2$$

$$v_3 = 20i_3$$

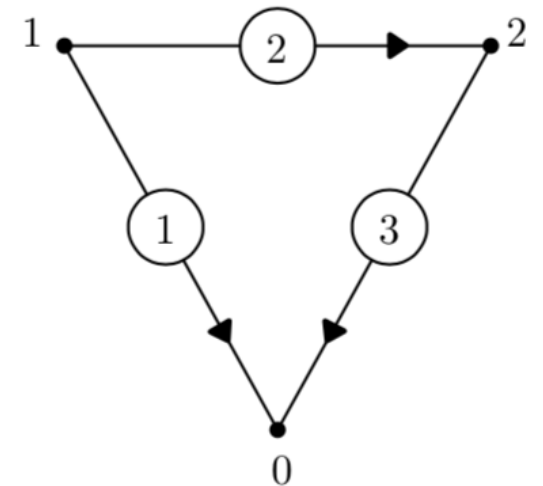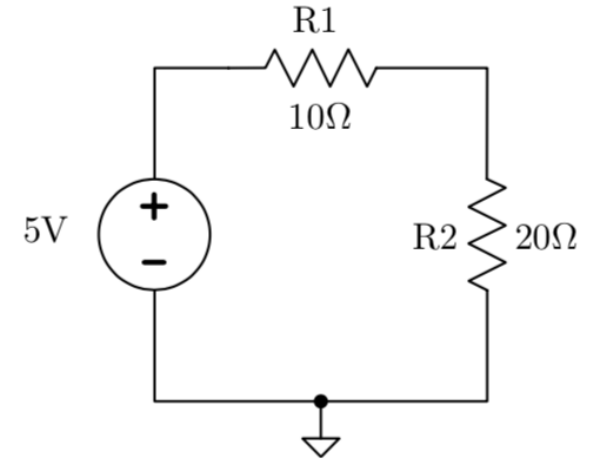

Step 2: From Netlist to Matrix

- (Continue) Represent these equations with matrices:

$$\begin{array}{l} v_1 = 5 \\ v_2 = 10i_2 \\ v_3 = 20i_3 \end{array} \quad \Rightarrow \quad \begin{array}{l} v_1 + 0i_1 = 5 \\ v_2 - 10i_2 = 0 \\ v_3 - 20i_3 = 0 \end{array} \quad \Rightarrow \quad \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} + \begin{bmatrix} 0 & 0 & 0 \\ 0 & -10 & 0 \\ 0 & 0 & -20 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{array}{ccc} \swarrow & \downarrow & \searrow \\ \text{voltages} & \text{currents} & \text{constants} \end{array}$$

Format: $av_b + bi_b = u_b$

$$\mathbf{M}\mathbf{v} + \mathbf{N}\mathbf{i} = \mathbf{u}_s$$

Step 3: Calculate Unknown Parameters

- Now, what do we have?

- KCL + KVL:

$$\begin{bmatrix} \mathbf{0} & \mathbf{0} & \mathbf{A} \\ -\mathbf{A}^T & \mathbf{1} & \mathbf{0} \end{bmatrix} \begin{bmatrix} \mathbf{e} \\ \mathbf{v} \\ \mathbf{i} \end{bmatrix} = \begin{bmatrix} \mathbf{0} \\ \mathbf{0} \end{bmatrix}$$

Ohm's Law:

$$\mathbf{M}\mathbf{v} + \mathbf{N}\mathbf{i} = \mathbf{u}_s$$

- Combine all the equations to create the sparse matrix representation:

$$\begin{bmatrix} \mathbf{0} & \mathbf{0} & \mathbf{A} \\ -\mathbf{A}^T & \mathbf{1} & \mathbf{0} \\ \mathbf{0} & \mathbf{M} & \mathbf{N} \end{bmatrix} \begin{bmatrix} \mathbf{e} \\ \mathbf{v} \\ \mathbf{i} \end{bmatrix} = \begin{bmatrix} \mathbf{0} \\ \mathbf{0} \\ \mathbf{u}_s \end{bmatrix} \quad \Rightarrow \quad \mathbf{T}\mathbf{w} = \mathbf{u}$$

Step 3: Calculate Unknown Parameters

$$\begin{bmatrix} \mathbf{0} & \mathbf{0} & \mathbf{A} \\ -\mathbf{A}^T & \mathbf{1} & \mathbf{0} \\ \mathbf{0} & \mathbf{M} & \mathbf{N} \end{bmatrix} \begin{bmatrix} \mathbf{e} \\ \mathbf{v} \\ \mathbf{i} \end{bmatrix} = \begin{bmatrix} \mathbf{0} \\ \mathbf{0} \\ \mathbf{u}_s \end{bmatrix}$$



Put everything we know
into the matrices

$$\left[\begin{array}{cc|ccc|ccc} 0 & 0 & 0 & 0 & 0 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1 \\ \hline -1 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ -1 & 1 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & -1 & 0 & 0 & 1 & 0 & 0 & 0 \\ \hline 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & -10 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & -20 \end{array} \right] \begin{bmatrix} e_1 \\ e_2 \\ \hline v_1 \\ v_2 \\ v_3 \\ \hline i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ \hline 0 \\ 0 \\ 0 \\ \hline 5 \\ 0 \\ 0 \end{bmatrix}$$

**Final goal: calculate
e, v, and i!**

Steps Review

1. Create a netlist as input to represent a circuit.
2. Use KCL, KVL and Ohm's law to construct three matrix equations.
 - Construct \mathbf{A} , \mathbf{M} , \mathbf{N} , and \mathbf{u}_s to represent the netlist.
3. Combine all the matrix equations to solve all the unknown parameters (e , v , i of each part).
 - Use Gauss Elimination, LU Factorization, etc.

Example 1

- Input:
 - V1 1 0 6
 - R1 1 2 6
 - R2 2 0 3.33
 - R3 2 3 3
 - R4 3 0 11
 - R5 3 4 4
 - R6 4 0 7
 - R7 4 5 7
 - R8 5 0 7

Example 1

- $A = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & -1 & 1 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1 \end{bmatrix}$

- $M = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}$

Input:

V1 1 0 6

R1 1 2 6

R2 2 0 3.33

R3 2 3 3

R4 3 0 11

R5 3 4 4

R6 4 0 7

R7 4 5 7

R8 5 0 7

Example 1

- $$\begin{aligned}
 & \begin{matrix} & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & & 6 \\ & 0 & -6 & 0 & 0 & 0 & 0 & 0 & 0 & & 0 \\ & 0 & 0 & -3.33 & 0 & 0 & 0 & 0 & 0 & & 0 \\ & 0 & 0 & 0 & -3 & 0 & 0 & 0 & 0 & & 0 \\ N = & 0 & 0 & 0 & 0 & -11 & 0 & 0 & 0 & & 0 \\ & 0 & 0 & 0 & 0 & 0 & -4 & 0 & 0 & & 0 \\ & 0 & 0 & 0 & 0 & 0 & 0 & -7 & 0 & & 0 \\ & 0 & 0 & 0 & 0 & 0 & 0 & 0 & -7 & & 0 \\ & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & -7 & 0 \end{matrix} & \mathbf{u_s} = & \begin{matrix} 6 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{matrix}
 \end{aligned}$$

Input:

V1 1 0 6

R1 1 2 6

R2 2 0 3.33

R3 2 3 3

R4 3 0 11

R5 3 4 4

R6 4 0 7

R7 4 5 7

R8 5 0 7

Thank you!

Readings:

- Excursion 1 Description