EEL 4837Programming for Electrical Engineers II

Qiangeng Yang Teaching Assistant

Department of Electrical and Computer Engineering
University of Florida at Gainesville

Excursion 2 – Technology Mapping

Reading:

- Excursion 2 Description

Logic Gate


- Logic gate
 - A device that acts as a building block for digital circuits.
 - One or more inputs (0/1) and only one output (0/1).
 - Performing a specific logic function.
- Some basic logic gates:

Name	NOT Ā		AND AB			NAND AB			OR A+B			NOR			XOR A ⊕ B			XNOR A⊕B O−		
Alg. Expr.																				
Symbol			<u>A</u> x																	
Truth	A	X	В	A	X	В	A	X	В	A	X	В	A	X	В	A	X	В	A	X
Table	0	1	0	0	0	0	0	1	0	0	0	0	0	1	0	0	0	0	0	
	1	0	0	1	0	0	1	1	0	1	1	0	1	0	0	1	1	0	1	
			1	0	0	1	0	1	1	0	1	1	0	0	1	0	1	1	0	
			1	1	1	1	1	0	1	1	1	1	1	0	1	1	0	1	1	

Logic Synthesis

Logic synthesis

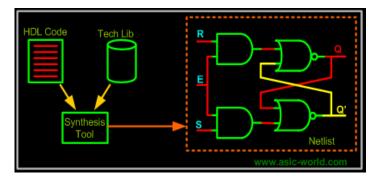
- The process of automatic production of logic components, in particular digital circuits.
- It includes:
 - Logic optimization
 - Simplifies logic expressions theoretically.
 - Technology mapping
 - Implements logic gates with physical layouts.
 - The topic of Excursion 2



Source: http://www.asic-world.com/verilog/synthesis1.html

Technology Mapping


Suppose we have these gates in our "library":

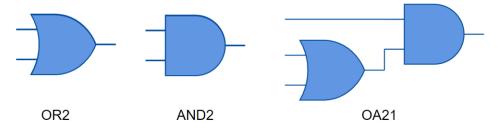

OA21: OR-AND, a so-called complex gate.

Number like 2 and 21: the count of direct inputs.

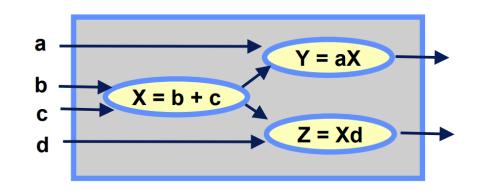
Suppose we need to build a model as follows:




Q: How can we realize it by using the gates in our library?

Technology Mapping

• Library:

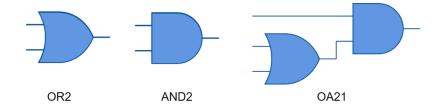


Model:

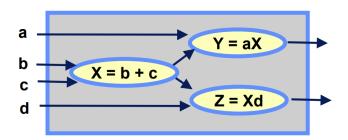


Solutions:

Solution 1: suppose we have all what we need :)

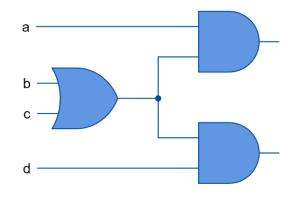


Solution 2: suppose we only have OA21:(

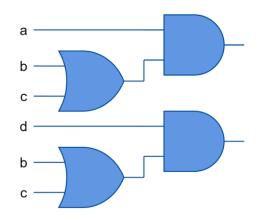

Excursion 2

- Goal:
 - Implement a tool for technology mapping.
 - Convert the original logic expressions into NAND and NOT gates.
 - Compute the minimal cost.
- General steps:
 - 1. Read a Boolean netlist.
 - 2. Convert the original structure into a NAND-NOT tree.
 - 3. Recursively compute the minimal cost.

Step 1: Read a Boolean netlist

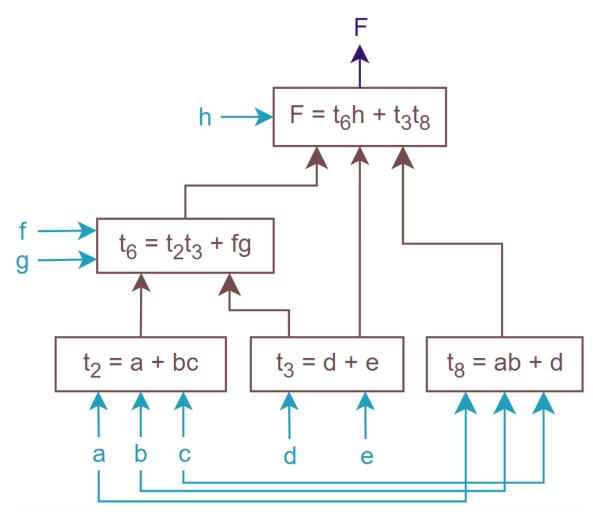


Note: some middle steps were combined only for elegance.

Netlist format:

```
t8 = OR t7 d
a INPUT
b INPUT
                      = AND t3 t8
                   t10 = AND t6 h
c INPUT
d INPUT
                   F = OR t9 t10
e INPUT
f INPUT
g INPUT
h INPUT
F OUTPUT
t1 = AND b c
t2 = OR a t1
t3 = OR d e
t4 = AND f g
t5 = AND t2 t3
t6 = OR t4 t5
t7 = AND a b
```

Step 2: Conversion into a NAND-NOT tree

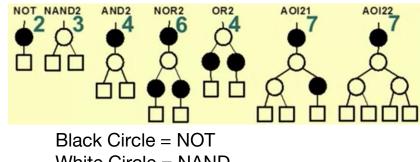
- Only NAND and NOT gates are available.
- Represent a gate of AND/OR/NOT by NANDs and NOTs only.
 - Transforming equations (De Morgan's laws):
 - NOT A = NOT A
 - A AND B = NOT (A NAND B)
 - A OR B = (NOT A) NAND (NOT B)



White Circle = NOT White Square = input


• Best practice: topologically traverse from output to input.

Library:

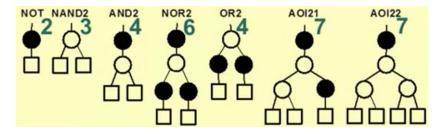


Black Circle = NOT White Circle = NAND White Square = input Number: cost


Consider a tree like this:

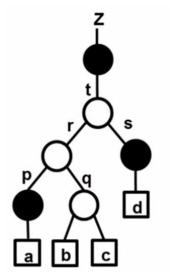

How can we describe the tree? What components provided in the library were used?

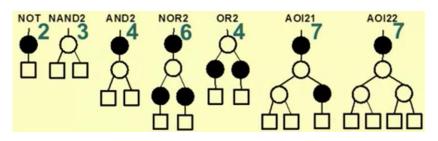
 Continue the recursion to compute the minimal cost at the other nodes.




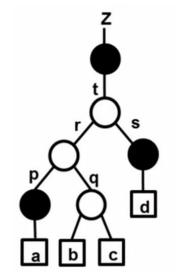

```
At node Can Match
                    With min cost
         NOT
                     2 + mincost(t)
         AND2
                     4 + mincost(r) + mincost(s)
                    (7 + mincost(p) + mincost(q)
         AOI21
                     3 + mincost(r) + mincost(s)
         NAND2
                     3 + mincost(p) + mincost(q)
         NAND2
                     2
         NOT
         NAND2
        NOT
```

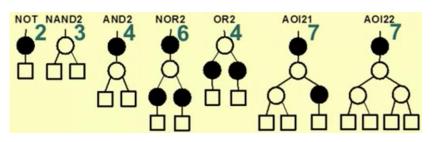
 Continue the recursion to compute the minimal cost at the other nodes.




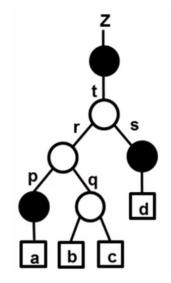



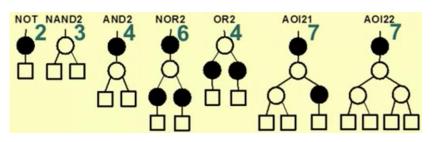
 Continue the recursion to compute the minimal cost at the other nodes.




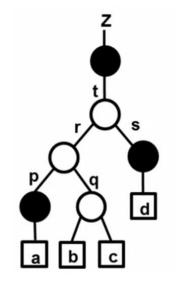




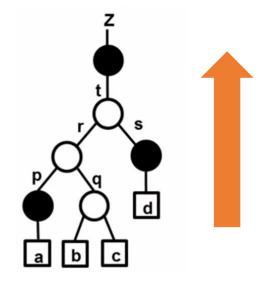
- (Optional, the other ways, bonus points)
 - Bottom-up
 - Dynamic programming




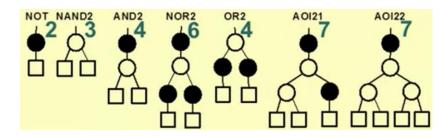

Return the calculated optimal cost.

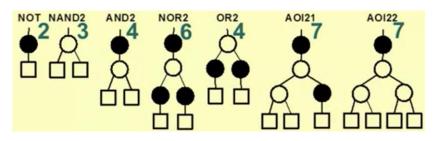

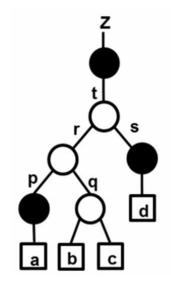

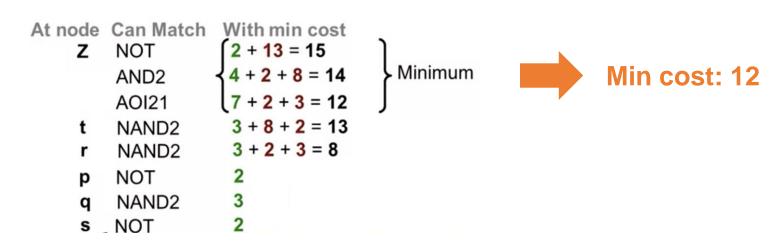

Quick Review

- Goal:
 - Implement a tool for technology mapping.
 - Convert the original expressions into NAND and NOT gates.
 - Compute the minimal cost.
- General steps:
 - 1. Read a Boolean netlist.
 - 2. Convert the original structure into a NAND-NOT tree.
 - 3. Recursively compute the minimal cost.

Thank you!

Reading:

- Excursion 2 Description